

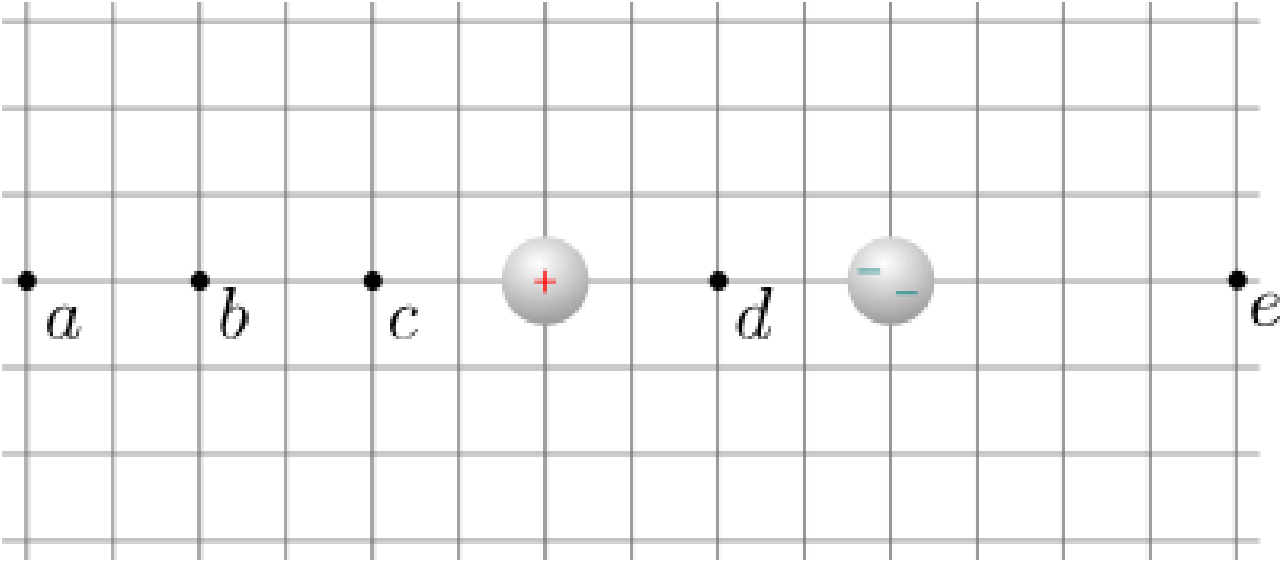


Which point has zero electric potential?

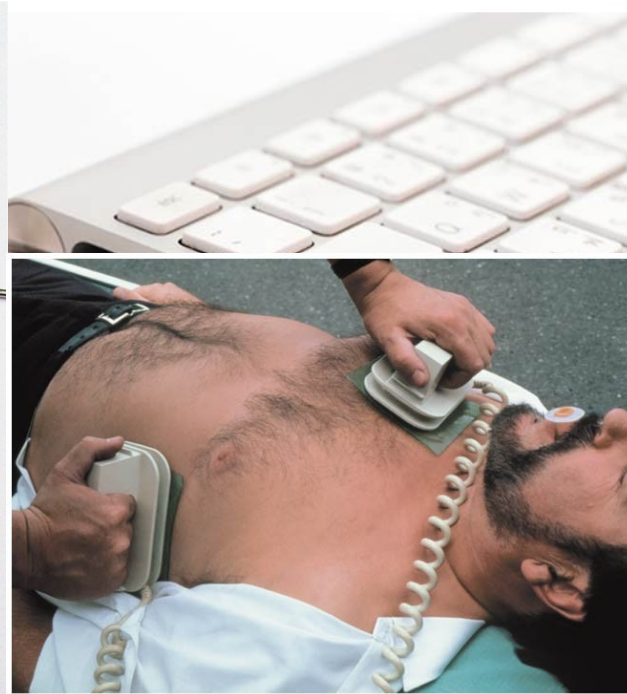

Chapter 8: Capacitance

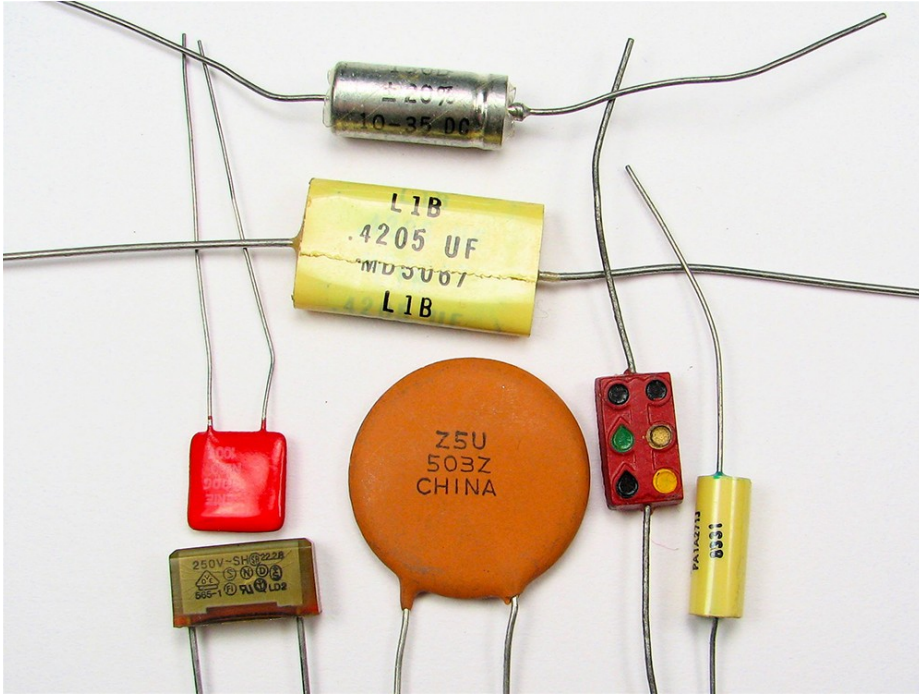


- 1 Capacitors and Capacitance
- 2 Capacitors in Series and in Parallel
- 3 Energy Stored in a Capacitor

- 4 Capacitor with a Dielectric
- 5 Molecular Model of a Dielectric


Capacitance and Capacitors

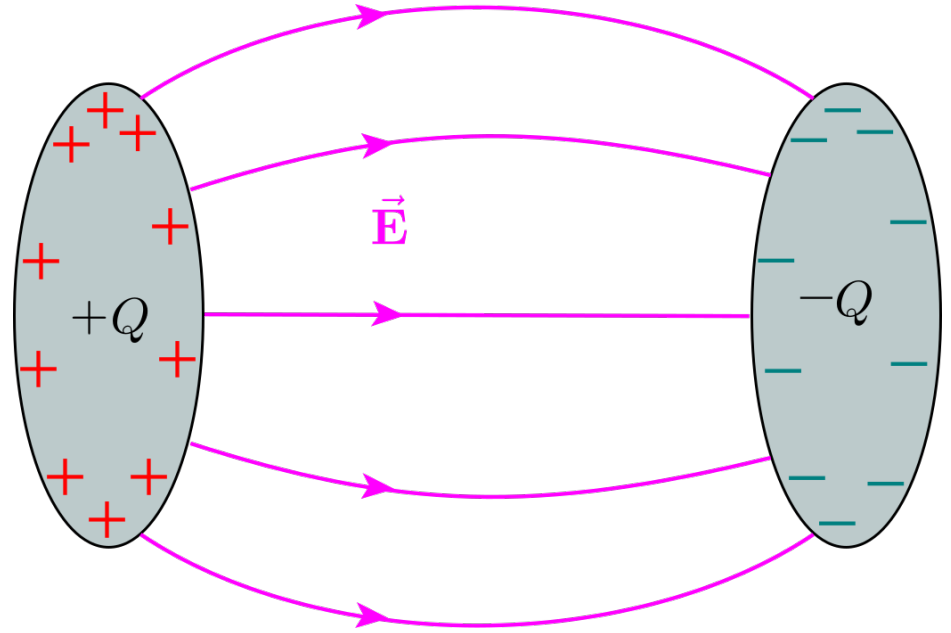- Separating charge Q onto two “electrodes” creates a potential difference ΔV between them




Capacitance and Capacitors

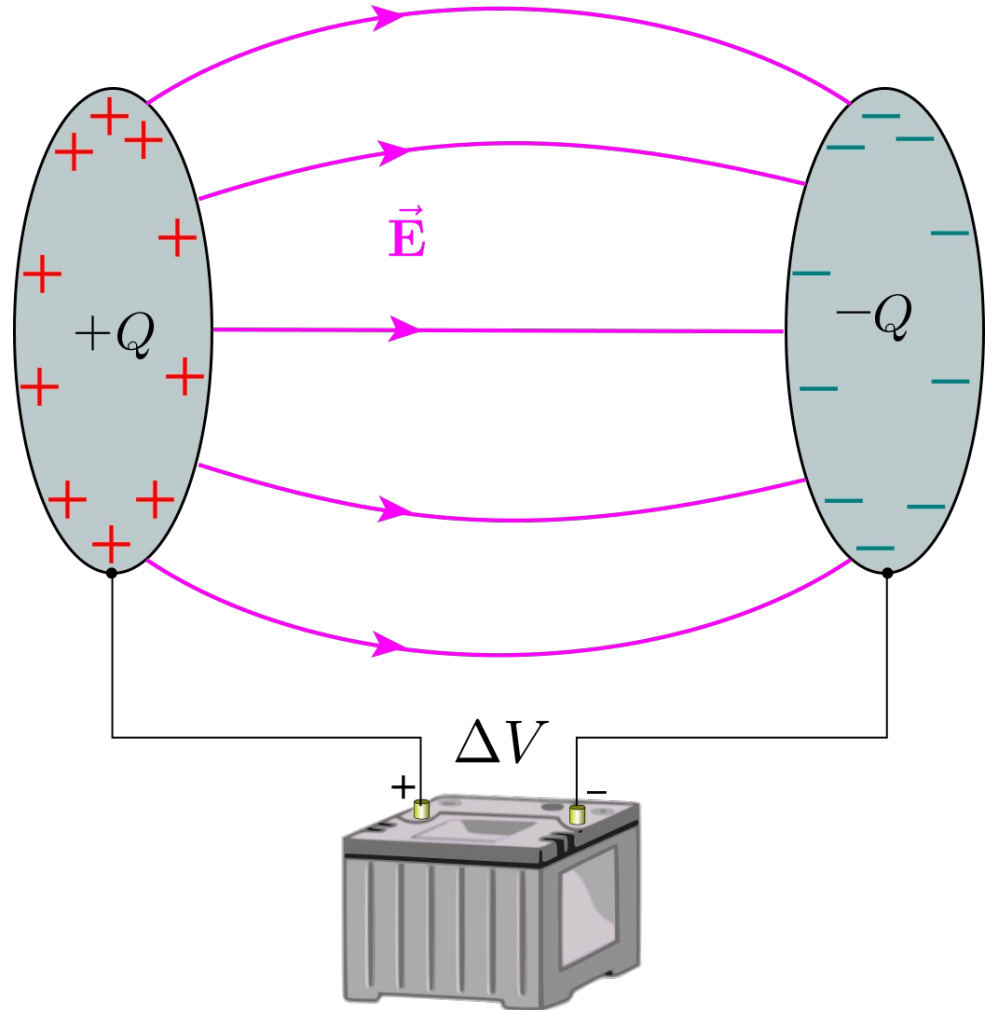- A voltage source (like a battery) does work on charges to move them
- The voltage source maintains a constant ΔV between the electrodes




Capacitance and Capacitors

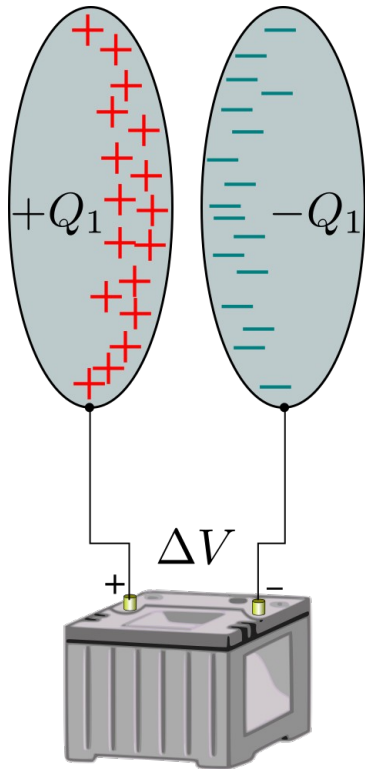The amount of charge Q that voltage ΔV can separate depends on the geometry of the electrodes




$$Q_1 > Q_2$$

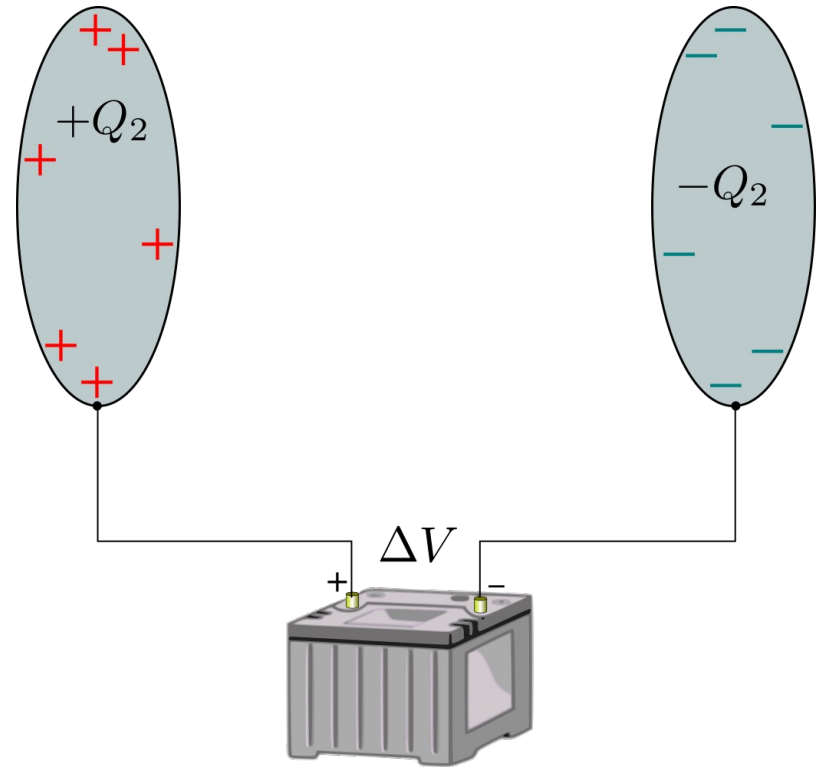


Capacitance and Capacitors

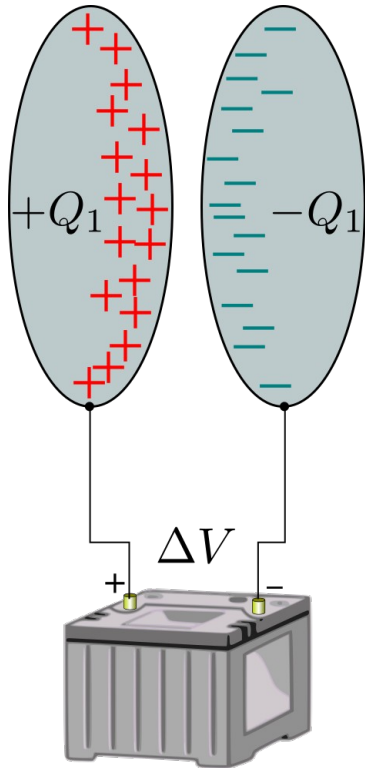The parallel-plate capacitor can store a lot of charge per volt applied.



$$Q_3 > Q_1$$

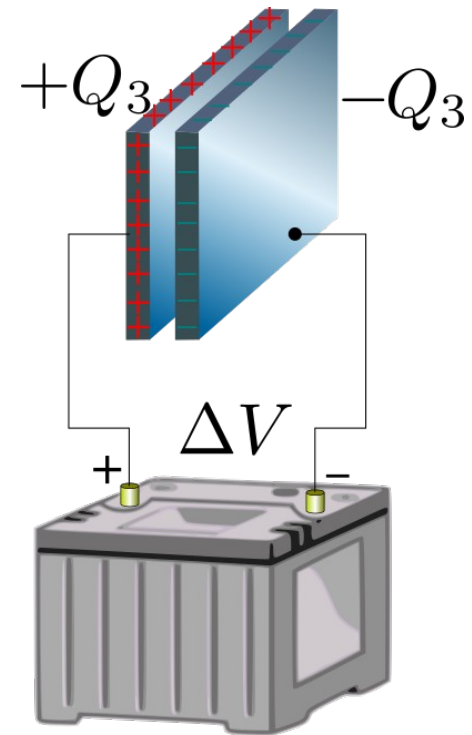


Capacitance and Capacitors

- The amount of charge per volt that a pair of electrodes can store is called its “capacitance”.

$$C = \frac{Q}{\Delta V}$$

- unit: Farads (F) $1\text{F} = 1 \frac{\text{C}}{\text{V}}$

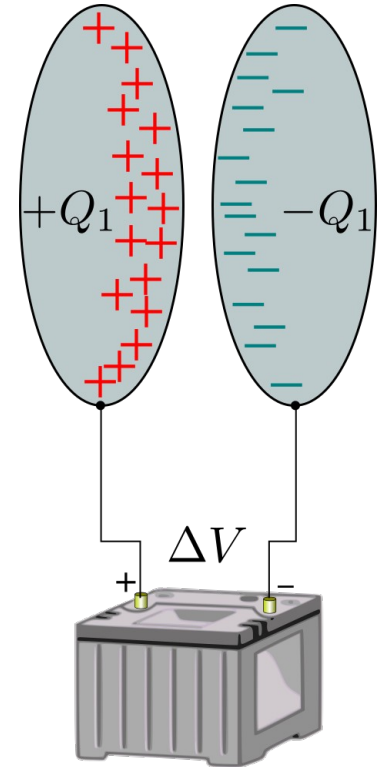- Capacitance depends on physical configuration of the conductors, not on Q or ΔV




Capacitance and Capacitors


Derive the capacitance of a parallel-plate capacitor

$$\begin{aligned}\Delta V &= - \int_i^f E ds \\ &= - \int_i^f \frac{\sigma}{\epsilon_0} ds = - \frac{\sigma}{\epsilon_0} d = - \frac{Q}{A\epsilon_0} d\end{aligned}$$



$$C = \frac{\epsilon_0 A}{d}$$

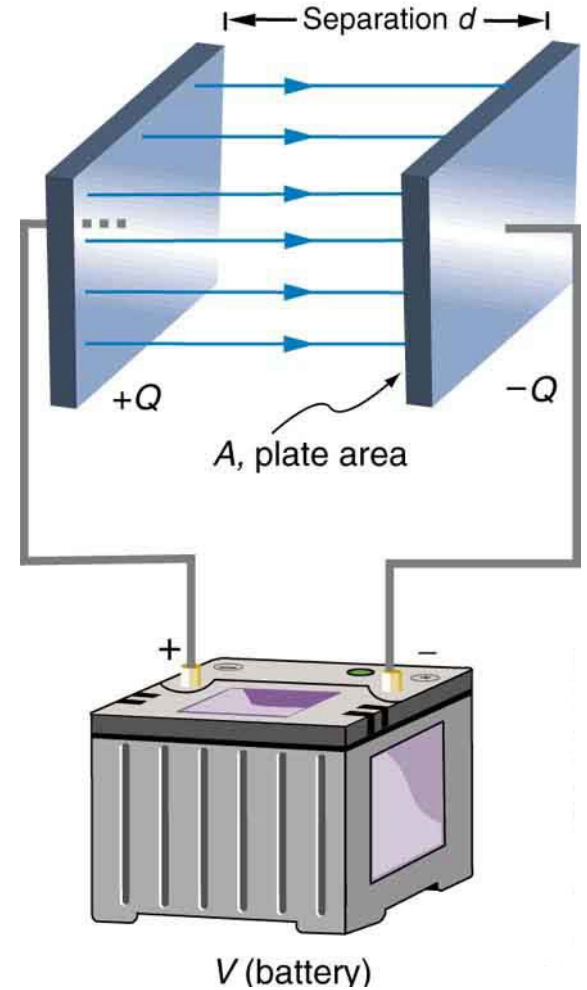


Capacitance and Capacitors

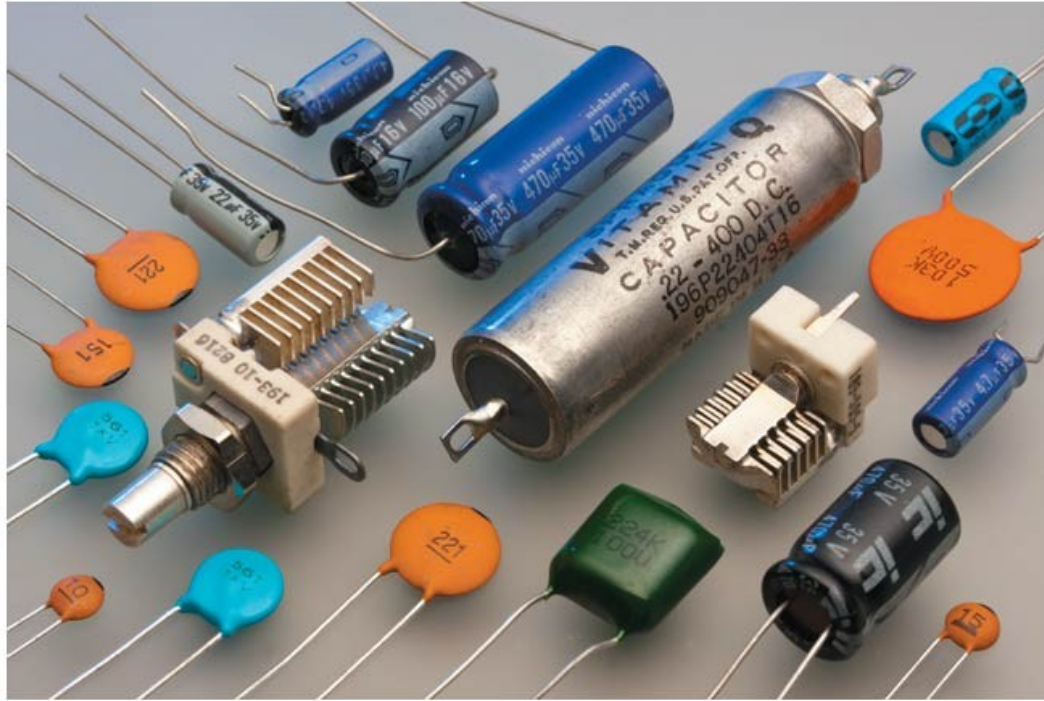

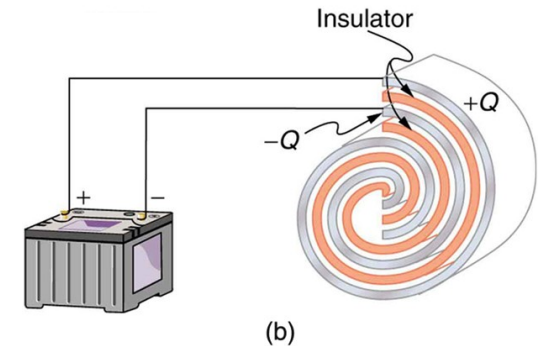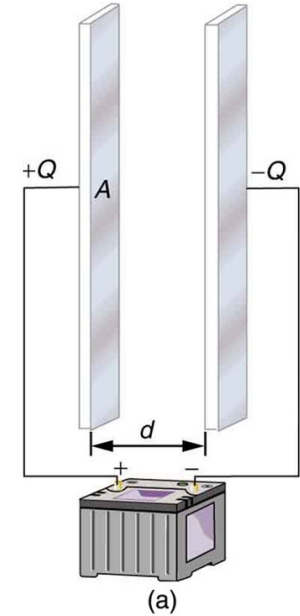Capacitors come in a variety of sizes and shapes.




Capacitance and Capacitors

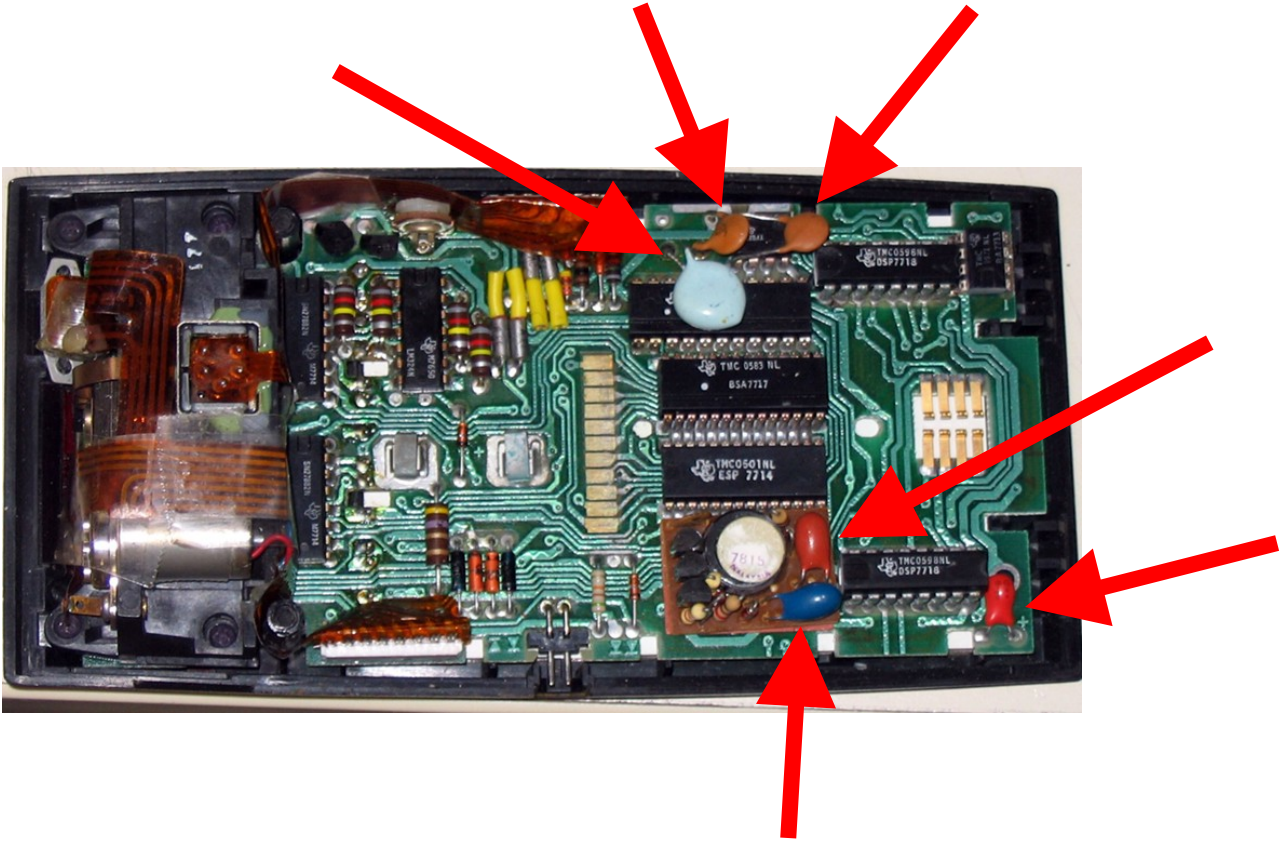


Capacitance and Capacitors

This is a variable capacitor

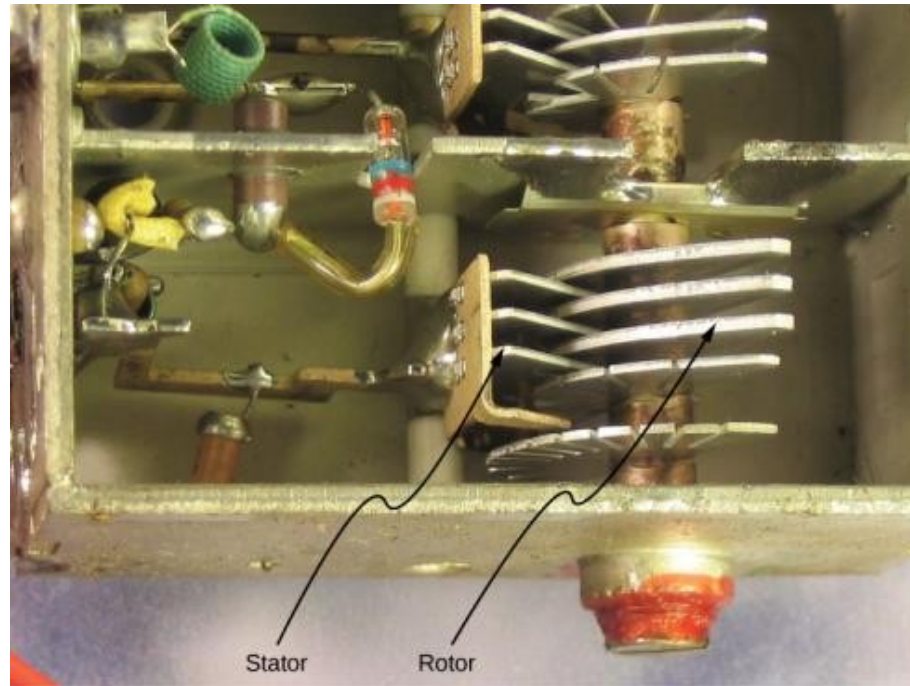


Circuit Diagrams

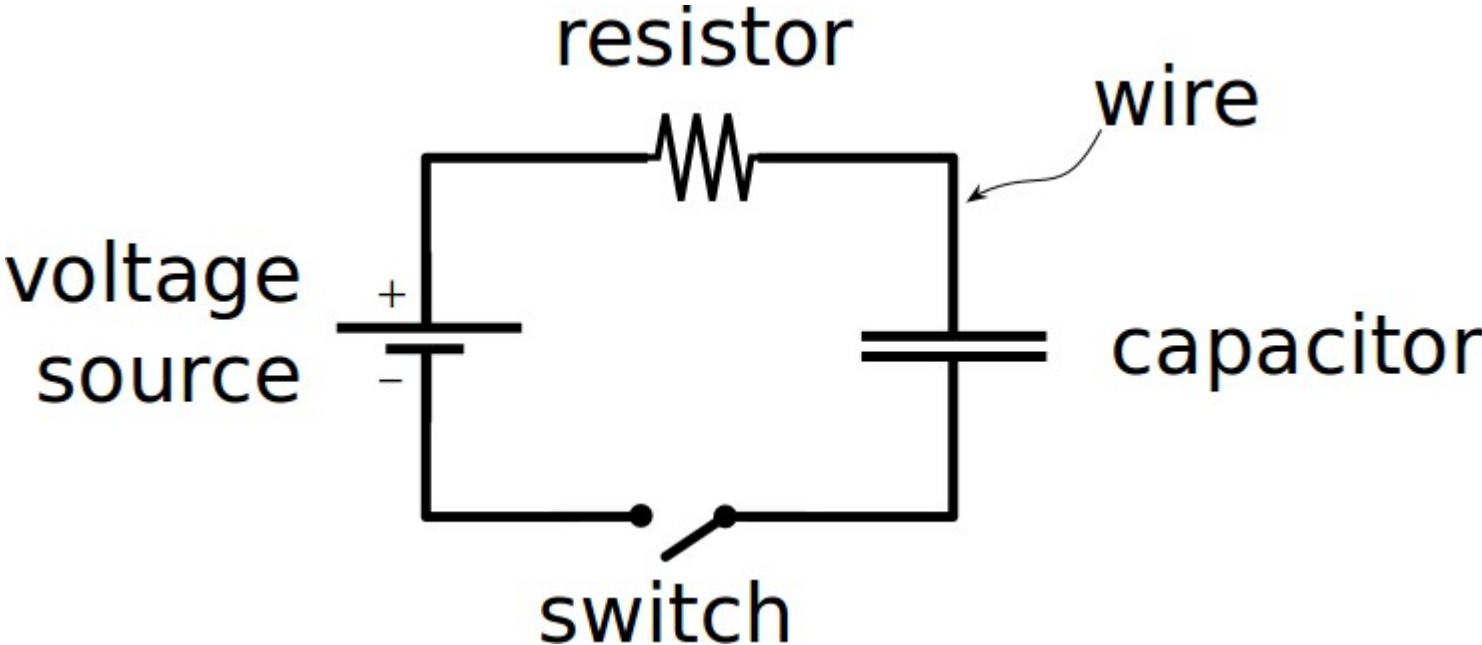

Circuit Diagrams


Capacitor Sim

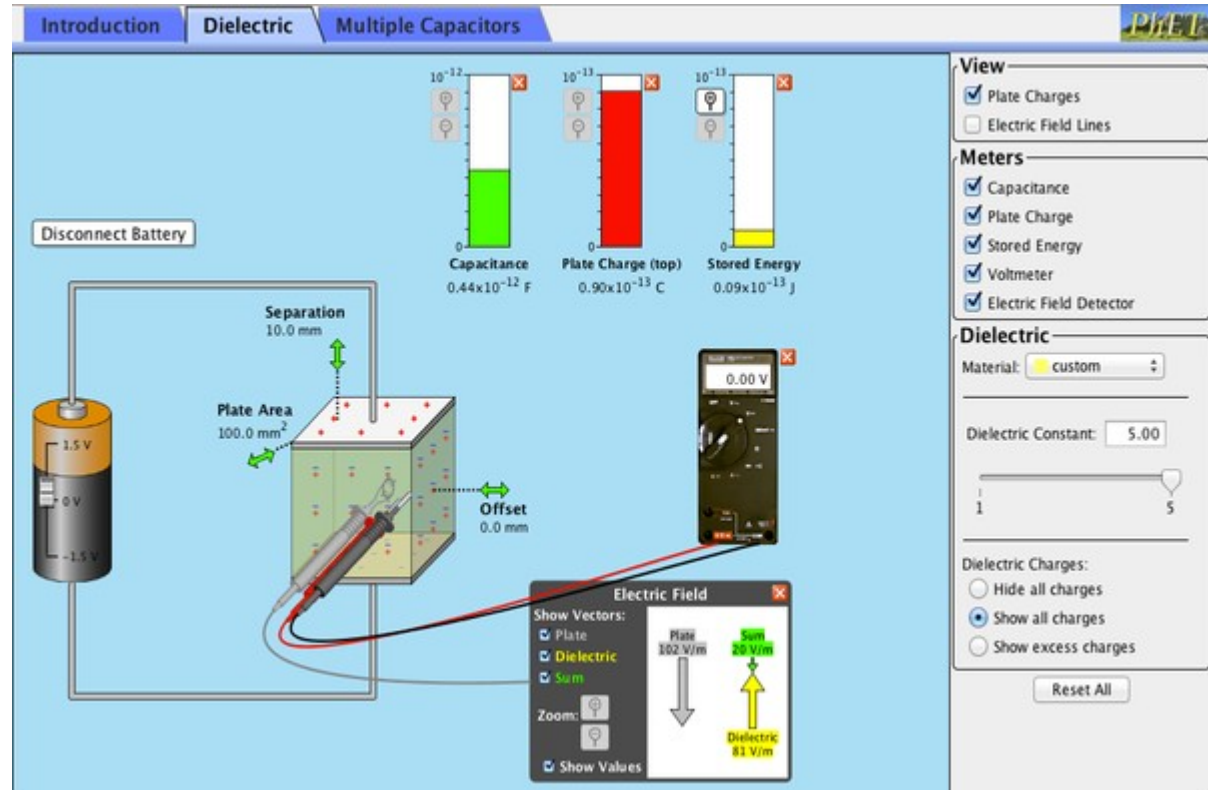

<https://phet.colorado.edu/en/simulation/legacy/capacitor-lab>


Capacitors in Combination

parallel capacitors

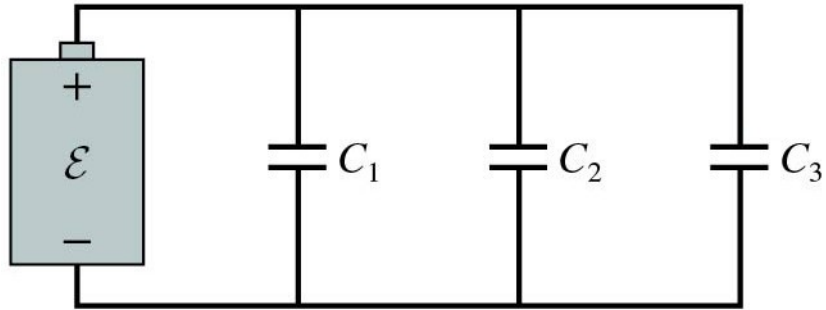

$$V_{\text{total}} = V_1 = V_2 = V_3$$

series capacitors

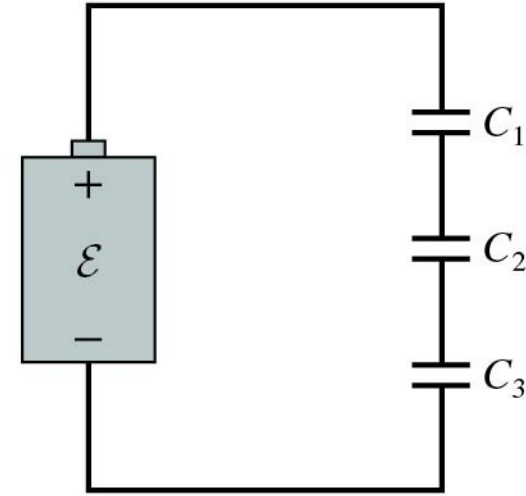



$$V_{\text{total}} = V_1 + V_2 + V_3$$

Capacitors in Combination

- Two capacitors C_1 and C_2 connected in parallel.
- The total charge drawn from the battery is $Q = Q_1 + Q_2$.
- We can replace the capacitors with a single “equivalent” capacitor:

$$C_{\text{eq}} = \frac{Q}{\Delta V_C} = \frac{Q_1 + Q_2}{\Delta V_C} = \frac{Q_1}{\Delta V_C} + \frac{Q_2}{\Delta V_C}$$


$$C_{\text{eq}} = C_1 + C_2$$

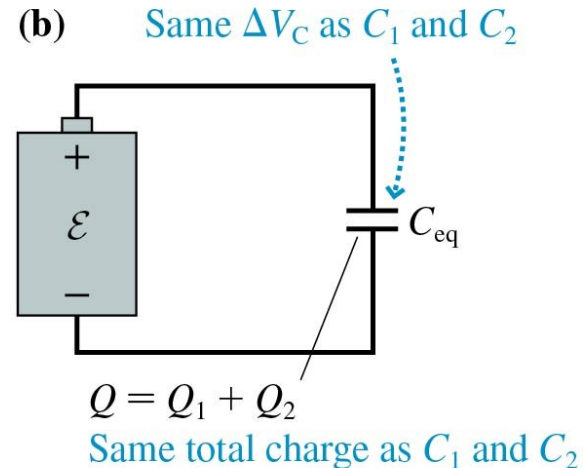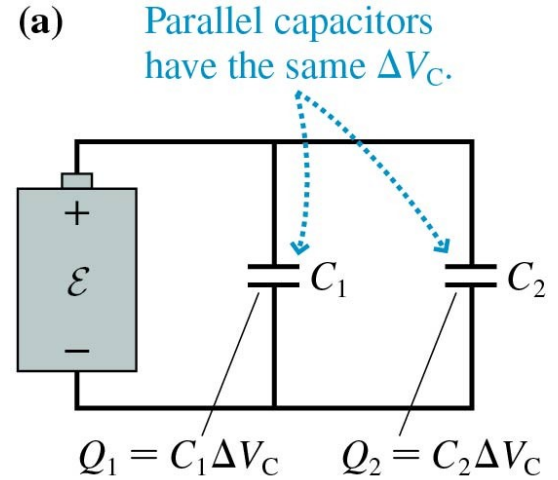

Capacitors in Combination

If capacitors C_1 , C_2 , C_3 , ... are in parallel, their equivalent capacitance is:
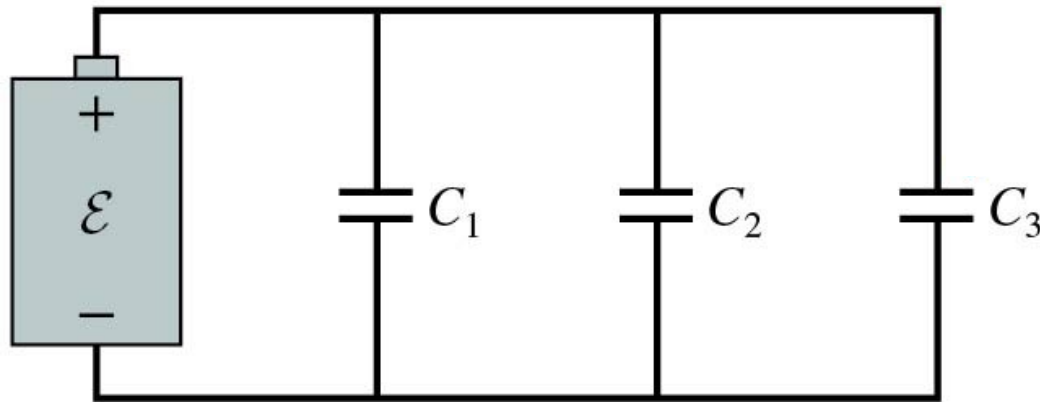
$$C_{\text{eq}} = C_1 + C_2 + C_3 + \dots \quad (\text{parallel capacitors})$$



Capacitors in Combination


- two capacitors C_1 and C_2 connected in series.
- The total potential difference across both capacitors is

$$\Delta V_C = \Delta V_1 + \Delta V_2.$$


- The inverse of the equivalent capacitance is

$$\frac{1}{C_{\text{eq}}} = \frac{\Delta V_C}{Q} = \frac{\Delta V_1 + \Delta V_2}{Q} = \frac{\Delta V_1}{Q} + \frac{\Delta V_2}{Q} = \frac{1}{C_1} + \frac{1}{C_2}$$

(a) Series capacitors have the same Q .

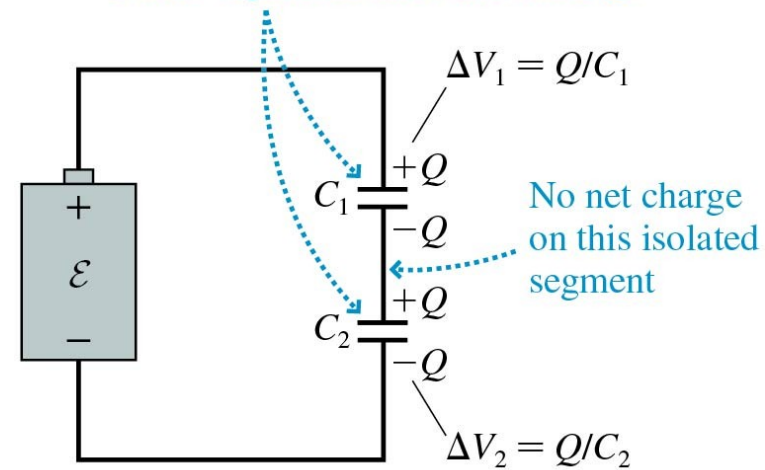


(b) Same Q as C_1 and C_2

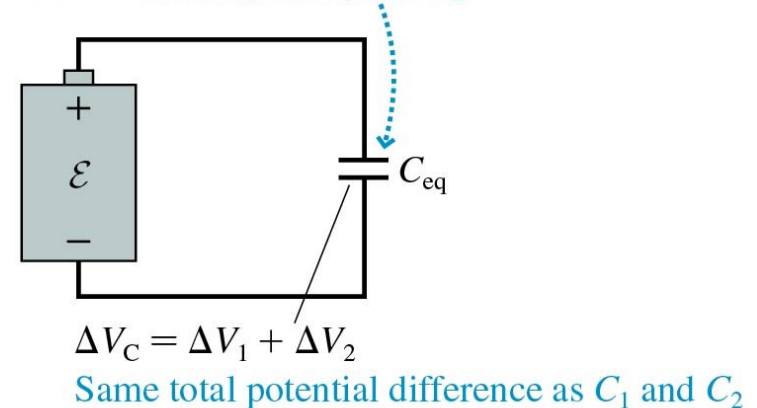

Capacitors in Combination

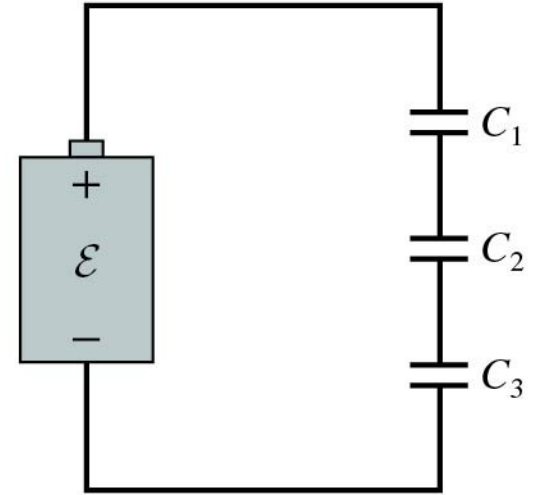
If capacitors C_1 , C_2 , C_3 , ... are in series, their equivalent capacitance is



$$C_{\text{eq}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \right)^{-1} \quad (\text{series capacitors})$$

Capacitors in Combination

Connected in parallel

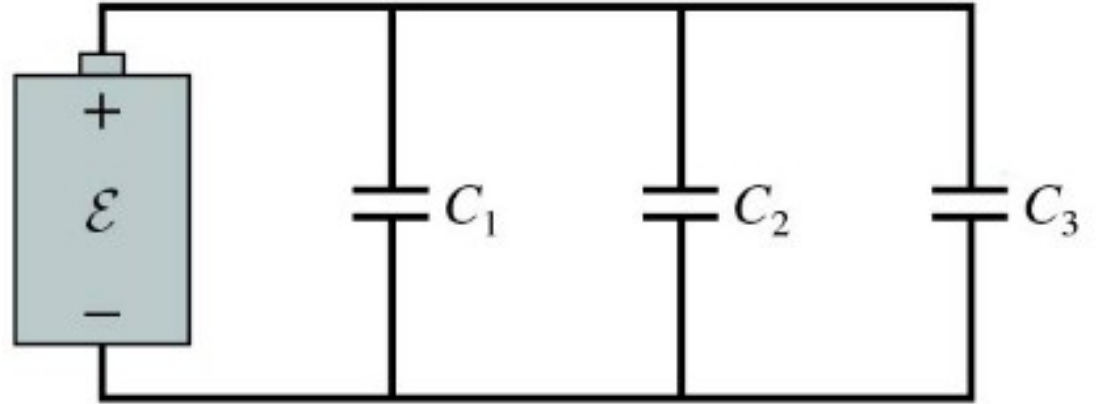

$$C_{\text{eq}} = C_1 + C_2 + C_3 + \dots$$

$$Q_{\text{total}} = Q_1 + Q_2 + Q_3 + \dots$$

$$V_{\text{total}} = V_1 = V_2 = V_3$$


Capacitors in Combination

Connected in series

$$C_{\text{eq}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \right)^{-1}$$

$$Q_{\text{total}} = Q_1 = Q_2 = Q_3$$

$$V_{\text{total}} = V_1 + V_2 + V_3$$

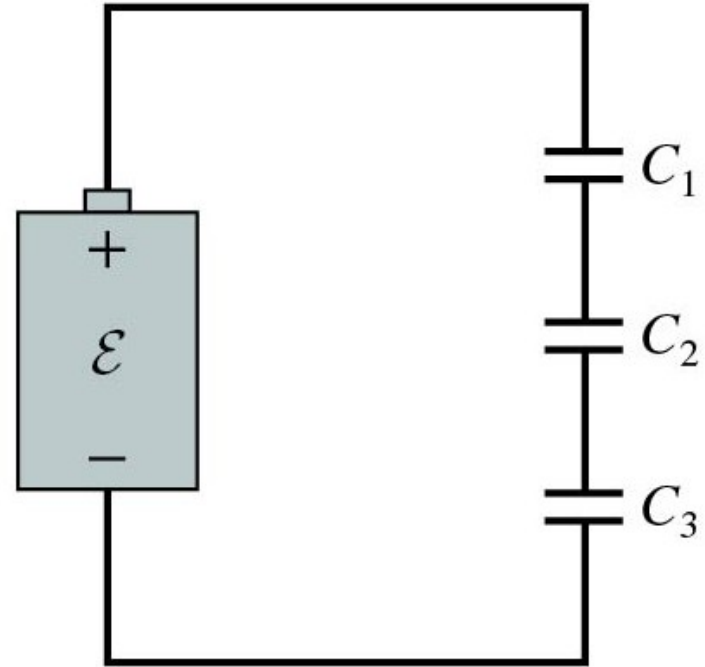


Capacitors in Combination

Which network has the greatest capacitance?


a.




b.

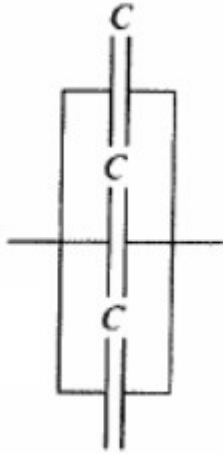

c.

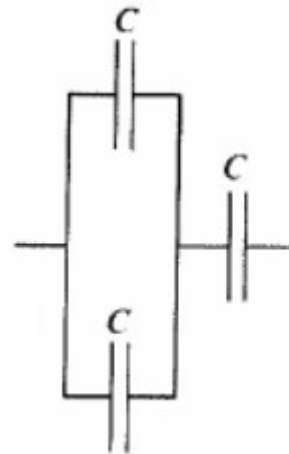

d.

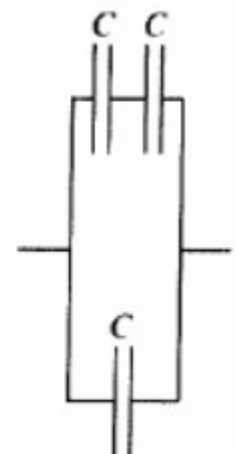


Energy Stored in a Capacitor

- As a small charge dq is lifted to a higher potential, the potential energy of the capacitor increases by

$$dU = dq \Delta V = \frac{q dq}{C}$$


- The total energy transferred from the battery to the capacitor is
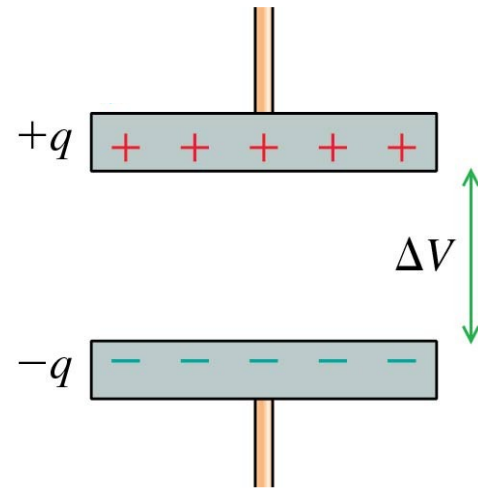
$$U_C = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C}$$



Energy Stored in a Capacitor
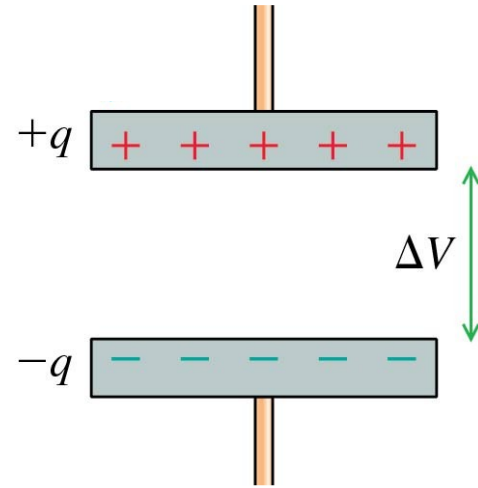
$$U_C = \frac{Q^2}{2C} = \frac{1}{2}C(\Delta V_C)^2$$



Energy Stored in a Capacitor

How much energy is stored in a $220 \mu\text{F}$ camera-flash capacitor that has been charged to 330 V ? What is the average power dissipation if this capacitor is discharged in 1.0 ms ?

$$U_C = \frac{1}{2} C (\Delta V_C)^2 = \frac{1}{2} (220 \times 10^{-6} \text{ F}) (330 \text{ V})^2 = 12 \text{ J}$$


$$P = \frac{\Delta E}{\Delta t} = \frac{12 \text{ J}}{1.0 \times 10^{-3} \text{ s}} = 12,000 \text{ W}$$

Energy Stored in a Capacitor

- The **energy density** of an electric field, such as the one inside a capacitor, is:

$$u_E = \frac{\text{energy stored}}{\text{volume in which it is stored}} = \frac{U_C}{Ad} = \frac{\epsilon_0}{2} E^2$$

- units J/m^3 .

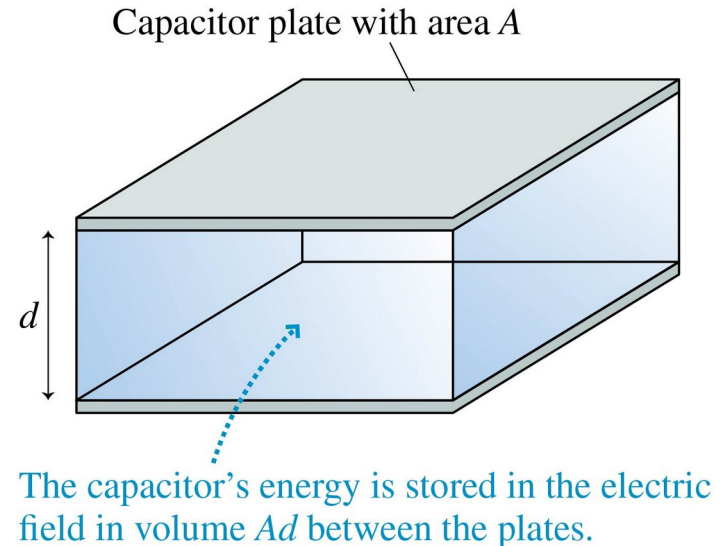

Energy Stored in a Capacitor

Capacitors are used in devices that need to store a lot of electrical energy for quick delivery




automated external defibrillator (AED)




camera flash

Dielectrics

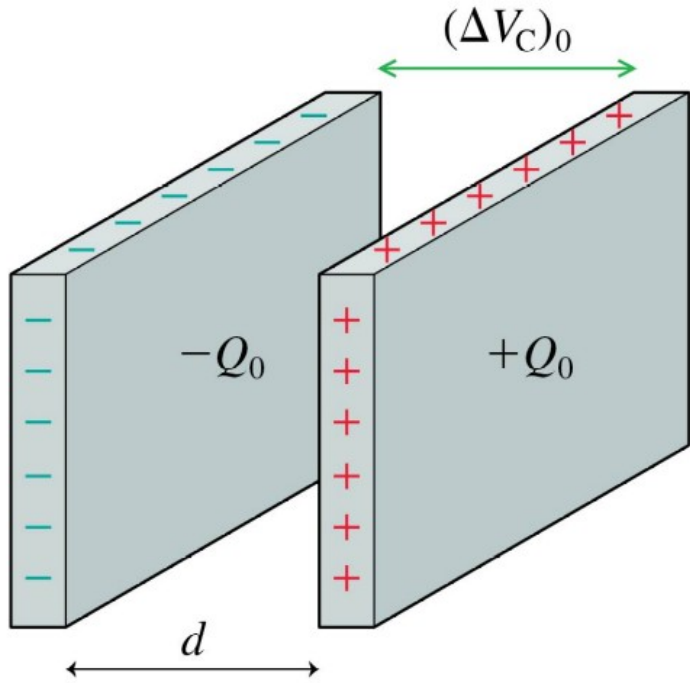

Capacitance C_0 in vacuum

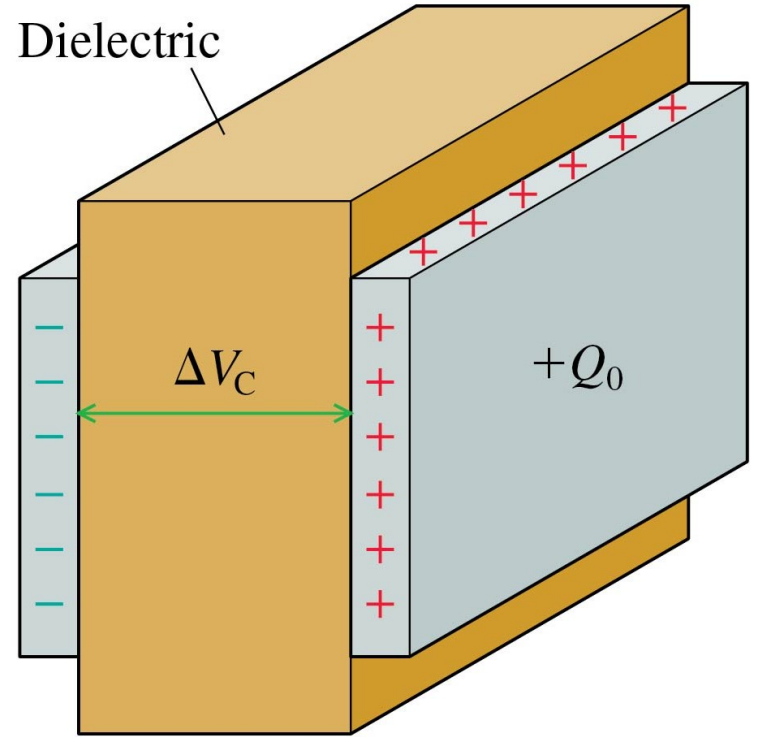


Capacitance $C > C_0$

$$C = \kappa C_0$$

Dielectrics

- The charge on the capacitor plates does not change ($Q = Q_0$).
- However, the voltage has *decreased*:





$$\Delta V_C < (\Delta V_C)_0$$

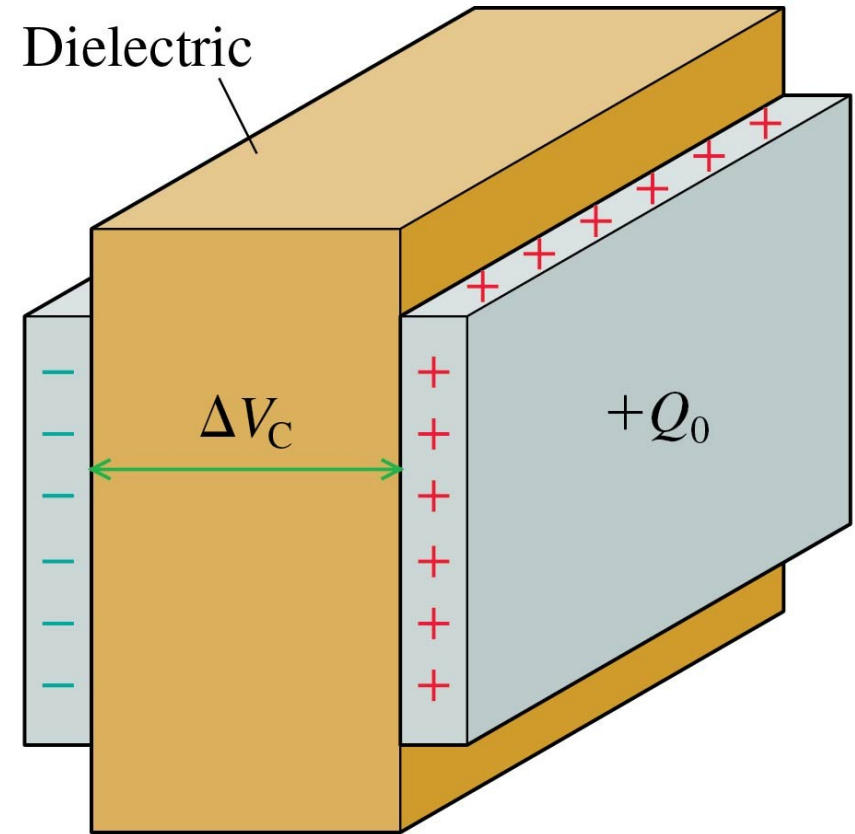

Capacitance $C > C_0$

Dielectrics

The insulator is polarized.

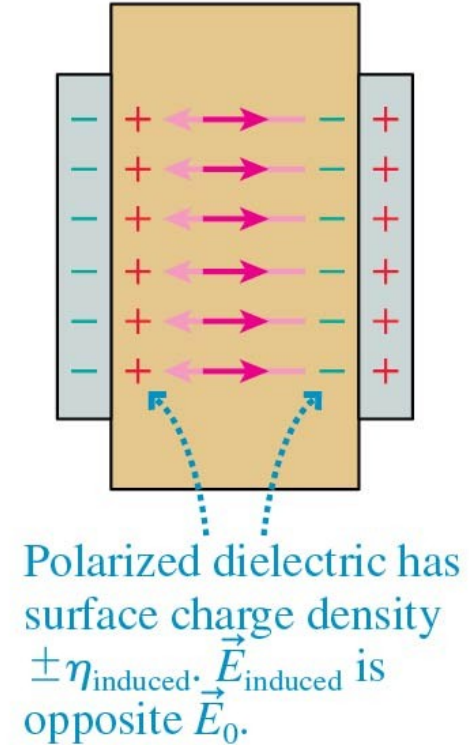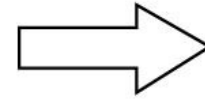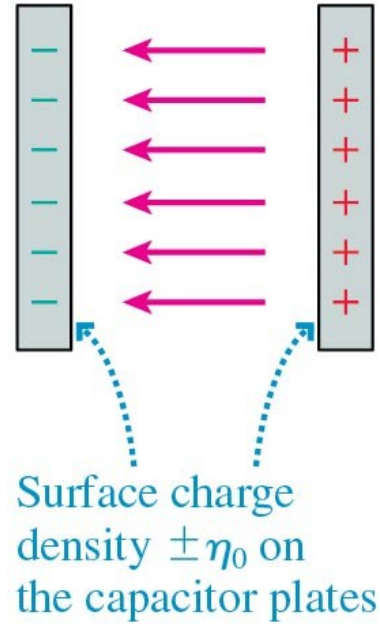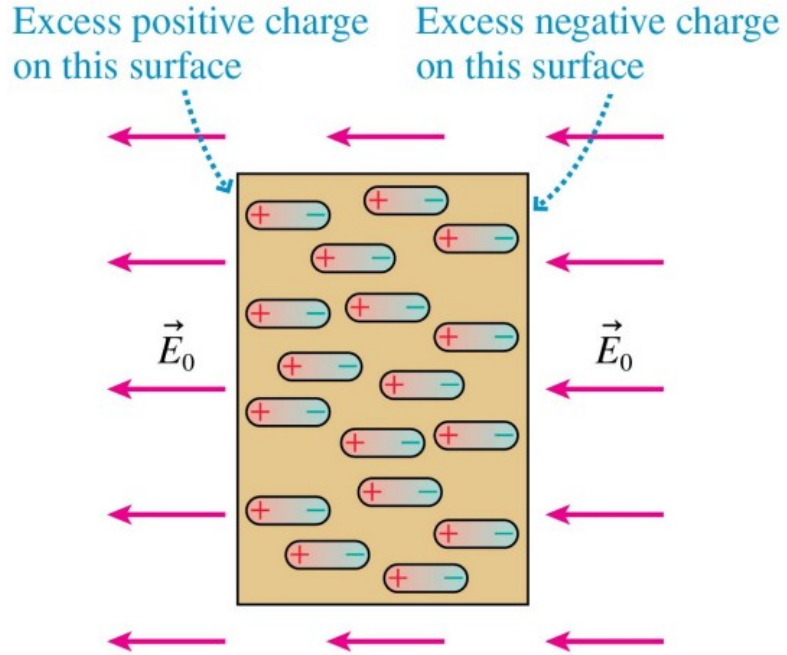


Dielectrics

- the **dielectric constant**: $\kappa \equiv \frac{E_0}{E}$
- Easily polarized materials have larger dielectric constants than materials not easily polarized.
- Vacuum has $\kappa = 1$ exactly.
- **Filling a capacitor with a dielectric increases the capacitance by a factor equal to the dielectric constant:**

$$C = \frac{Q}{\Delta V_C} = \frac{Q_0}{(\Delta V_C)_0 / \kappa} = \kappa \frac{Q_0}{(\Delta V_C)_0} = \kappa C_0$$

Dielectrics

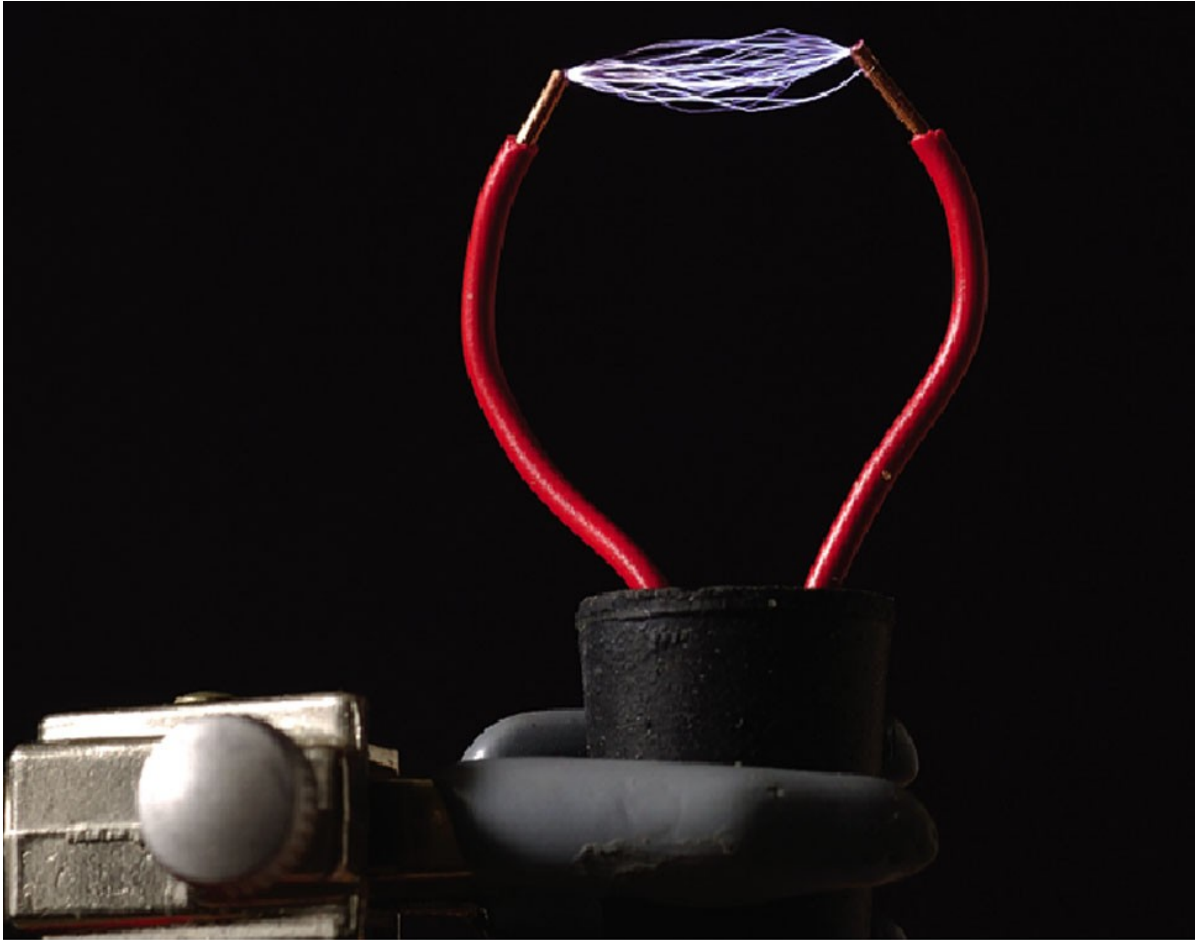

Material	Dielectric constant κ	Dielectric strength E_{\max} (10^6 V/m)
Vacuum	1	—
Air (1 atm)	1.0006	3
Teflon	2.1	60
Polystyrene plastic	2.6	24
Mylar	3.1	7
Paper	3.7	16
Pyrex glass	4.7	14
Pure water (20°C)	80	—
Titanium dioxide	110	6
Strontium titanate	300	8


Dielectrics

With voltage source connected: V is constant, Q can change

With *no* voltage source connected: Q is constant, V can change

C only changes with a physical change to the capacitor.

See simulation:

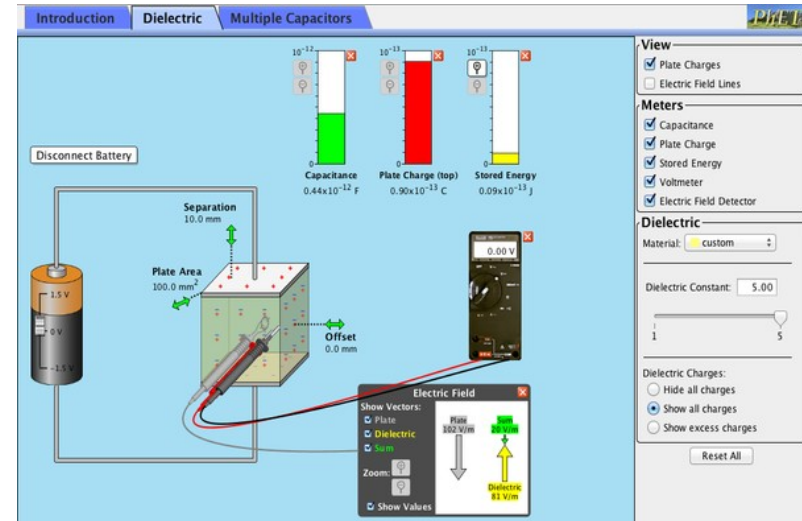

Dielectrics

A 5.0 nF parallel-plate capacitor is charged to 160 V. It is then disconnected from the battery and immersed in distilled water. What are (a) the capacitance and voltage of the water-filled capacitor and (b) the energy stored in the capacitor before and after its immersion?

$$C = \kappa C_0 = 80 \times 5.0 \text{ nF} = 400 \text{ nF}$$

At the same time, the voltage decreases to

$$\Delta V_C = \frac{(\Delta V_C)_0}{\kappa} = \frac{160 \text{ V}}{80} = 2.0 \text{ V}$$

$$(U_C)_0 = \frac{1}{2} C_0 (\Delta V_C)_0^2 = \frac{1}{2} (5.0 \times 10^{-9} \text{ F}) (160 \text{ V})^2 = 6.4 \times 10^{-5} \text{ J}$$

After being immersed, the stored energy is

$$U_C = \frac{1}{2} C (\Delta V_C)^2 = \frac{1}{2} (400 \times 10^{-9} \text{ F}) (2.0 \text{ V})^2 = 8.0 \times 10^{-7} \text{ J}$$